

Lab 6 Report

Huy Lai — 132000359

Kyle Crusius — 428003578

Arjun Kurkal — 631004597

Vishnu Naidu — 630004567

Texas A&M University

13 December 2022

An Aggie does not lie, cheat or steal.
Nor does an Aggie tolerate those who do.

Our Eternal thanks to **Kevin Weston** for helping us decipher this entire CPU.

Fetch

The Fetch stage reads the instructions from the instructions memory and places the arguments into `iCode`, `iFun`, `rA`, `rB`, and `valC`.

The `FetchRegEnable` sub-circuit will allow the Fetch stage to load the value `iCode`, `iFun`, `rA`, and `rB`. The `FetchDataEnable` sub-circuit will allow the Fetch state to load the value `valC`. Both of these circuits will also handle the varying lengths of instructions and load the appropriate bytes into the output.

The `FetchValP` sub-circuit will allow the Fetch state to load the value `valP`

Additionally, when the Fetch stage is done loading the instruction and its required values, a complete pulse is sent. Since the Fetch stage needs to load between one and 10 bytes, the complete flag, using `valP`, will dynamically wait until all the values are loaded.

Contributors

Huy Lai
Arjun Kurkal
Kevin Weston

Screenshots

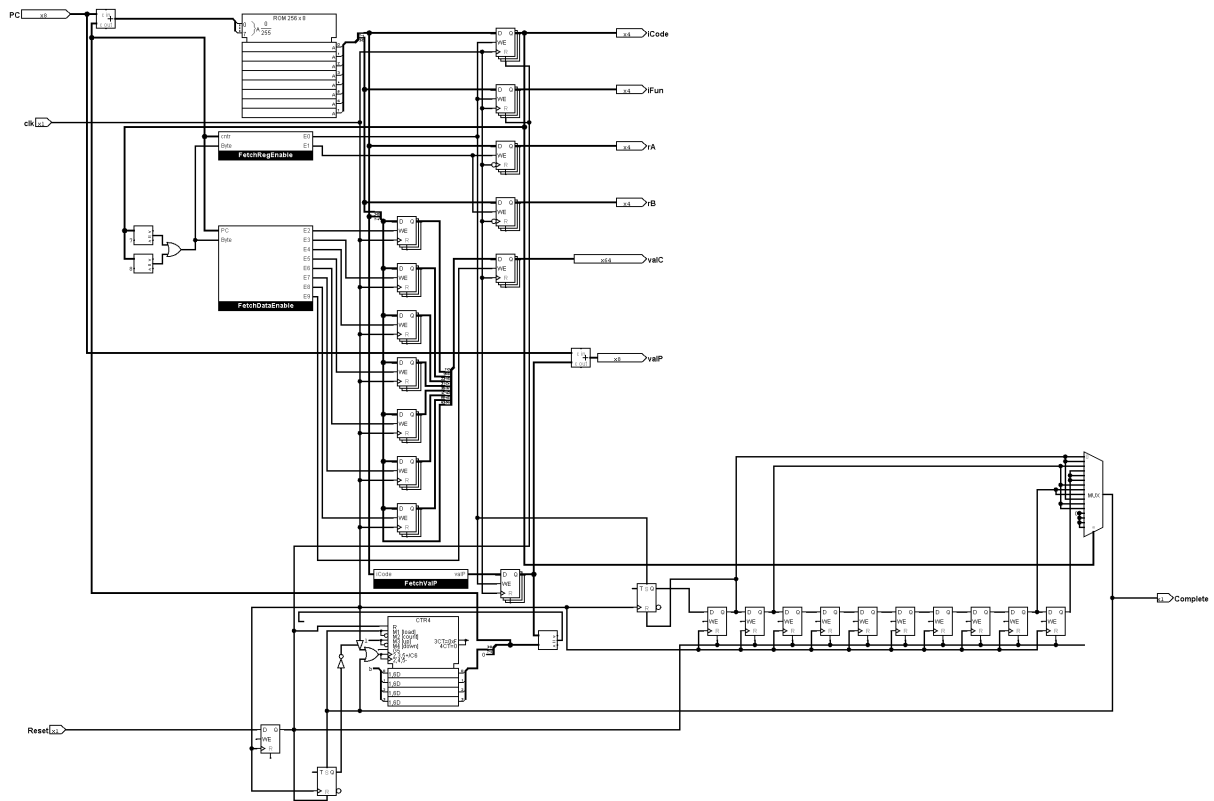


Figure 1: Fetch

Decode

The Decode block provides access to the register file, as well as interpreting instructions from Fetch to regulate read and access. The Decode block accepts `iCode`, `rA`, `rB`, `valM`, `valE`, `dstM`, and `dstE` as input (as well as a clock signal). It returns `valA` and `valB`.

Decode is comprised of three primary subsections: the register file, `srcA`, and `srcB`.

The register file provides output to `valA` and `valB` based on the registers it is instructed to read. Using `iCode`, `srcA` and `srcB` determine if a register needs to be read, and passes along the address from `rA` or `rB` respectively if so.

The register file can also be modified using `dstM`, `dstE`, `valM`, and `valE`. If the `WriteEnable` is enabled, the register file will update the corresponding destination with its appropriate value. The `MEDecoder` helps determine which of E or M should be written to, since only one can happen at a time.

Contributors

Kyle Crusius

Screenshots

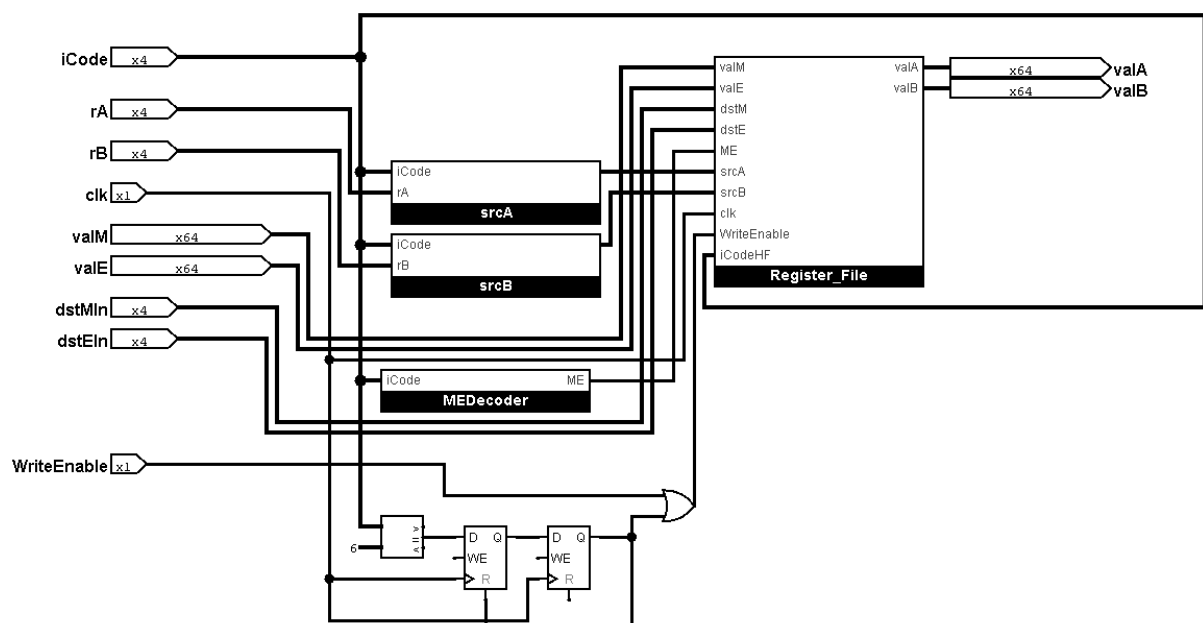


Figure 2: Decode

Execute

The Execute stage takes `iCode`, `iFun`, `valA`, `valB`, and `valC` along with the clock signal as inputs and outputs `valE`. Additionally, the Sign Flag, Overflow Flag, and the Zero Flag are set during this stage.

`iCode`, `valA`, `valB`, and `valC` are fed into `CTRLLogic`, which uses the information regarding the current instruction to send into the ALU the two values on which an operation is to be executed.

`ifun` and `icode` are fed into `ALUFun` to generate a 2 bit output, `noCodenoFun`, to communicate to the ALU which operation to execute.

The ALU takes in 3 inputs, `A`, `B`, and `notFun`, and computes the necessary operation (between addition, subtraction, logical AND, and logical XOR). The output is sent out to `ValE` and stored in a register, and the flags are set in `pcc`.

`setCC` takes in `iCode` in order to determine if the flag should be set on this operation or not. This output, along with both the clock and the flag outputs, are fed into `CC` in order to set the flag. This output is then used to set the jump condition in combination with `ifun`, to be used later in `PCUpdate`.

Contributors

Arjun Kurkal

Screenshots

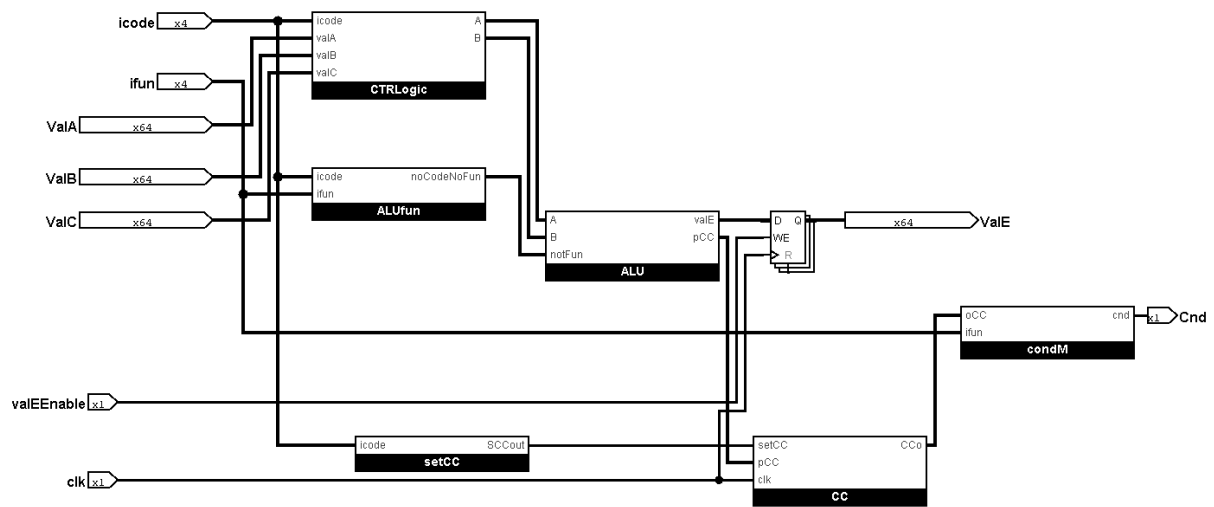


Figure 3: Execute

Memory

The Memory Stage take `iCode`, `valE`, `valA`, and `valP` as well as the clock signal and outputs `valM`. Additionally, when writing value into memory or reading values from memory, a `complete` pulse is send when the Memory Stage is doing doing so.

`Icode` is fed into `MemEnabler`, which outputs `oEnable`, `wEnable`, `rEnable`, `addrEnable`, and `datEnable`, which respectively communicate if any output is to be sent to `ValM`, if any value is to be written to RAM, if any value is to be read from RAM, whether the address for RAM access comes from `valE` or `valA`, and whether or not the write address comes from `valP` or `valA`.

This data is written to or read from RAM using a loop to read and write data byte for byte, which is handled with a counter that starts when the pulse enters the Memory stage. When that pulse reaches the end of memory, it signals to the next instruction that the memory stage is complete.

Contributors

Arjun Kural
Huy Lai

Screenshots

 


Figure 4: Memory

Write Back

The Write Back stage will allow for the writing to the register file. It takes `iCode`, `rA`, and `rB` as inputs and outputs `dstE` and `dstM`.

Contributors

Huy Lai
Arjun Kurkal

Screenshots

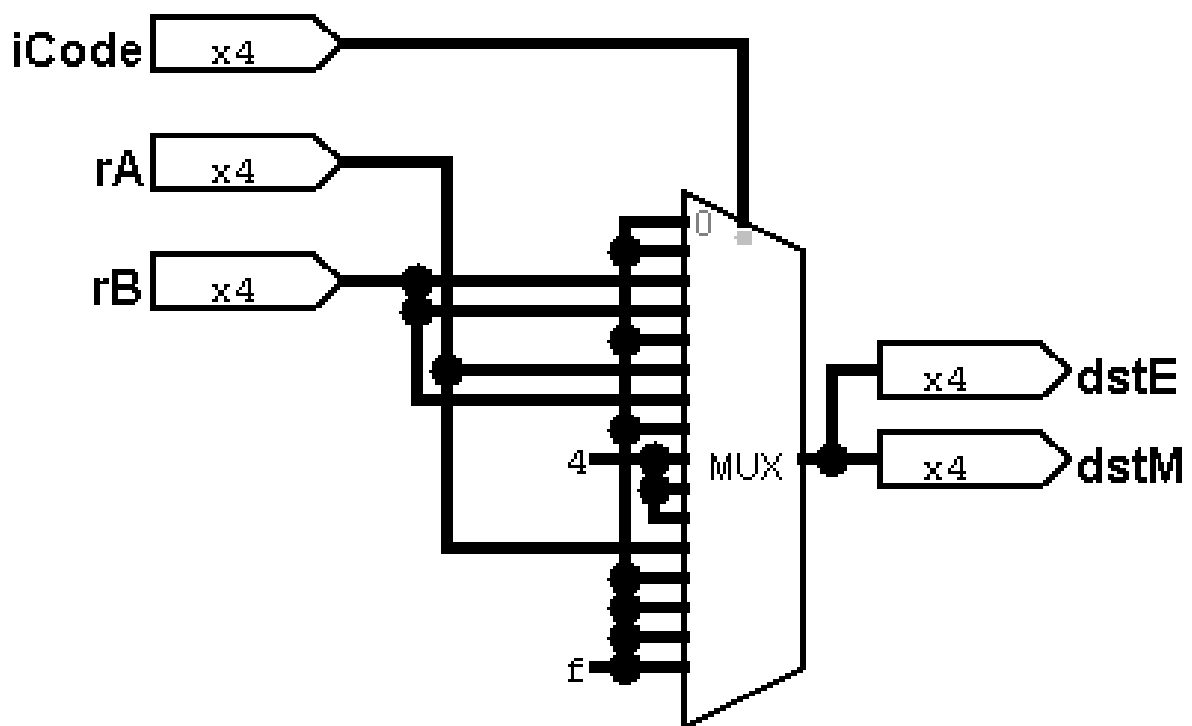


Figure 5: Write Back

PC Update

The PC Update stage will tell the PC where to go next. It takes `iCode`, `valP`, `valM`, `valC` along with `cnd` from the Execute stage as inputs. `cnd` is used on `jXX`, when high this indicates that a jump is being made.

Contributors

Huy Lai
Arjun Kurkal
Kyle Crusius

Screenshots

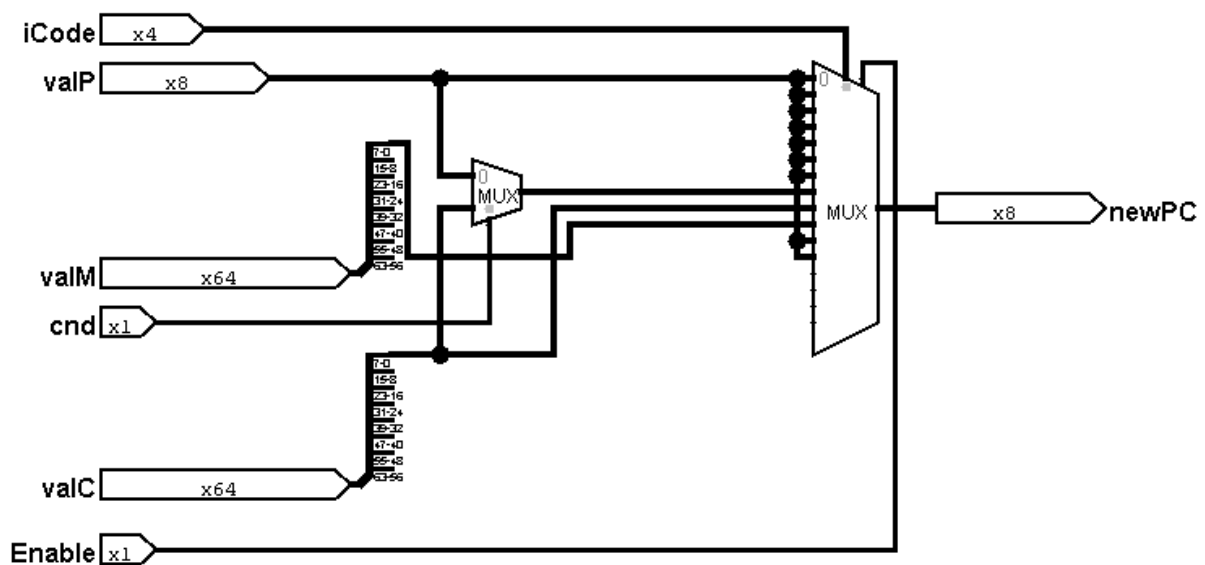


Figure 6: PC Update

Timing Diagrams

Because the timing diagrams are so long, they are split across multiple screen shots.

However each row of the image is always the same signal.

From top to bottom, there are:

- Clock
- iCode
- iFun
- rA
- rB
- valC
- valP
- valA
- valB
- valE
- valM
- (new) PC

[illegible][illegible]

The diagram illustrates a 16-bit bus system. At the top, a 16-bit data bus is shown with a sequence of bits: 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1 0. Below this, a 16-bit address bus is shown with the value 0000 1001. The CPU is connected to the data bus via a 16-bit data bus. The memory is connected to the data bus via a 16-bit data bus. The CPU is shown reading data from memory address 0000. The data bus shows the value 0000 0000 0000 0000. The address bus shows the value 0000 0000 0000 0000.

12

 


Figure 10: Call Test Part 4

OP Test

 


Figure 11: OP Test Part 1

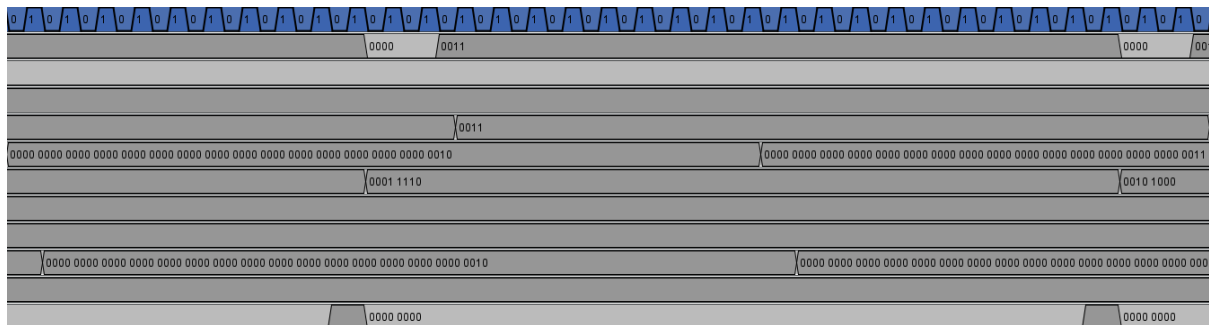


Figure 12: OP Test Part 2

 


Figure 13: OP Test Part 3

 


Figure 14: OP Test Part 4

 


Figure 15: OP Test Part 5

 


Figure 16: OP Test Part 6

[illegible][illegible]

The diagram illustrates a 16-bit bus system. The bus is represented by a horizontal bar with 16 segments, each containing a bit value (0 or 1). The bus is connected to a processor on the left and memory on the right. The processor has a data bus and a control bus. The memory has a data bus and a control bus. The diagram shows the bus being used to transfer data from memory to the processor. The data being transferred is 0000 0110. The control bus shows the processor sending a read signal to the memory.

16

[illegible][illegible][illegible]

17

